


190905514
MOHAMMAD TOFIK

WEE 8 LAB 8 :

1. Write and simulate the Verilog code to swap the contents of two registers using multiplexers.

```
module swapmux(X,Y,Xout,Yout);  
input X,Y;  
output Xout,Yout;  
wire M;  
mux2to1 mux1(Y,{~X,X},M);  
mux2to1 mux2(M,{~Y,Y},Yout);  
mux2to1 mux3(Yout,{~M,M},Xout);  
endmodule  
  
module mux2to1(S,W,f);  
input S;  
input [0:1]W;  
output f;  
assign f = S?W[1]:W[0];  
endmodule
```

OUTPUT :

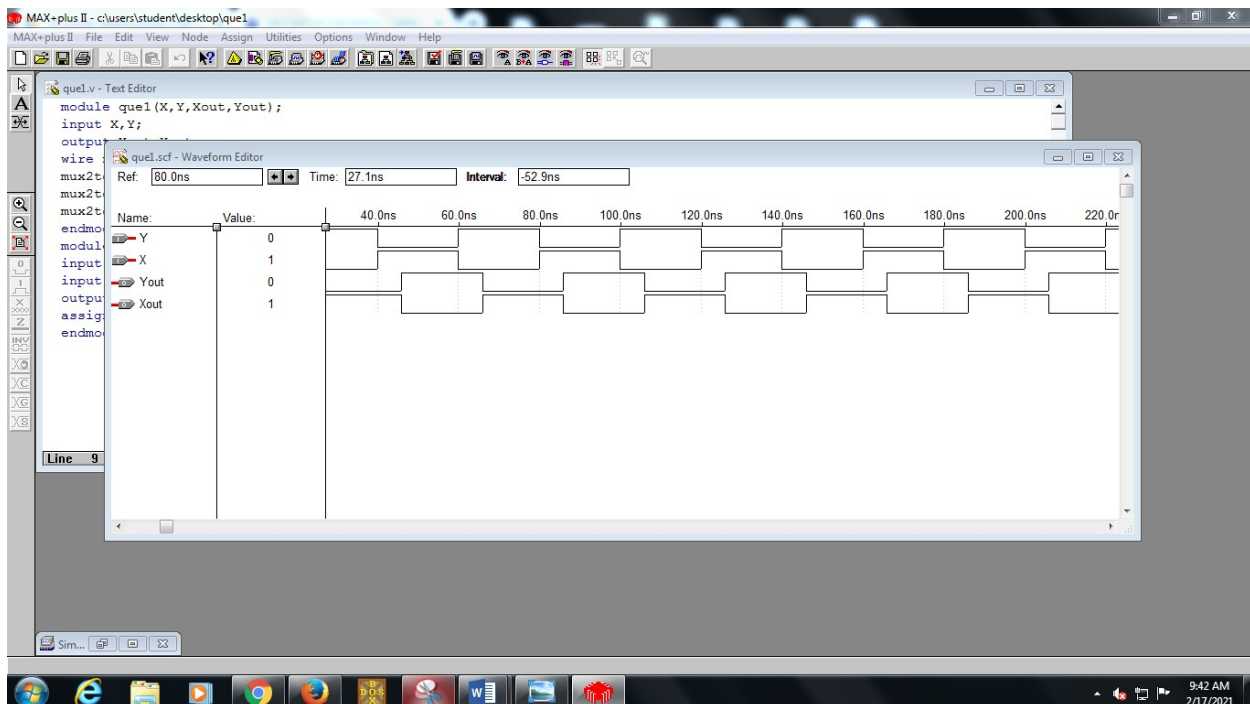

2. Simulate a simple processor that can perform the following functions:

```
module processor(Data, Reset, w, Clock, F, Rx, Ry, R0, R1, R2, R3,
Count, I, BusWires);
input [3:0] Data;
input Reset, w, Clock;
input [1:0] F, Rx, Ry;
output [1:0] Count, I;
output [3:0] BusWires, R0, R1, R2, R3;
reg [3:0] BusWires;
reg [3:0] Sum;
reg [0:3] Rin, Rout;
reg Extern, Ain, Gin, Gout, AddSub;
//wire [1:0] Count, I;
wire [0:3] Xreg, Y;
wire [3:0] A, G;
wire [1:6] Func, FuncReg, Sel;
upcount1 counter (Reset, Clock, Count);
assign Func = {F, Rx, Ry};
wire FRin = w & ~Count[1] & ~Count[0];
regn3 functionreg (Func, FRin, Clock, FuncReg);
//defparam functionreg.n = 6;
assign I = FuncReg[1:2];
dec2to4 decX (FuncReg[3:4], 1'b1, Xreg);
dec2to4 decY (FuncReg[5:6], 1'b1, Y);
always @(Count or I or Xreg or Y)
begin
Extern = 1'b0; Ain = 1'b0; Gin = 1'b0;
Gout = 1'b0; AddSub = 1'b0; Rin = 4'b0; Rout = 4'b0;
case (Count)
```

```

2'b00: ; //no signals asserted in time step T0
2'b01: //define signals in time step T1
case (I)
2'b00: begin //Load
Extern = 1'b1; Rin = Xreg;
end
2'b01: begin //Move
Rout = Y; Rin = Xreg;
end
default: begin //Add, Sub
Rout = Xreg; Ain = 1'b1;
end
endcase
2'b10: //define signals in time step T2
case(I)
2'b10: begin //Add
Rout = Y; Gin = 1'b1;
end
2'b11: begin //Sub
Rout = Y; AddSub = 1'b1; Gin = 1'b1;
end
default: ; //Add, Sub
endcase
2'b11:
case (I)
2'b10, 2'b11:
begin
Gout = 1'b1; Rin = Xreg;
end

```

```

default: ; //Add, Sub
endcase
endcase
end

regn2 reg_0 (BusWires, Rin[0], Clock, R0);
regn2 reg_1 (BusWires, Rin[1], Clock, R1);
regn2 reg_2 (BusWires, Rin[2], Clock, R2);
regn2 reg_3 (BusWires, Rin[3], Clock, R3);
regn2 reg_A (BusWires, Ain, Clock, A);
// alu
always @(AddSub or A or BusWires)
begin
if (!AddSub)
Sum = A + BusWires;
else
Sum = A - BusWires;
end

regn2 reg_G (Sum, Gin, Clock, G);
assign Sel = {Rout, Gout, Extern};
always @(Sel or R0 or R1 or R2 or R3 or G or Data)
begin
if (Sel == 6'b100000)
BusWires = R0;
else if (Sel == 6'b010000)
BusWires = R1;
else if (Sel == 6'b001000)
BusWires = R2;
else if (Sel == 6'b000100)
BusWires = R3;

```

```

else if (Sel == 6'b000010)
    BusWires = G;
else BusWires = Data;
end
endmodule

```

```

module upcount1(Clear, Clock, Q);
input Clear, Clock;
output [1:0] Q;
reg [1:0] Q;
always @(posedge Clock)
    if (Clear)
        Q <= 0;
    else
        Q <= Q + 1;
endmodule

```

```

module regn2(R, L, Clock, Q);
parameter n = 4;
input [n-1:0] R;
input L, Clock;
output[n-1:0] Q;
reg [n-1:0] Q;
always @(posedge Clock)
    if (L)
        Q <= R;
endmodule

```

```

module dec2to4 (W, En, Y);
input [1:0]W;

```

```

input En;
output [0:3] Y;
reg [0:3] Y;
always @(W or En)
case ({En,W})
3'b100: Y = 4'b1000;
3'b101: Y = 4'b0100;
3'b110: Y = 4'b0010;
3'b111: Y = 4'b0001;
default: Y = 4'b0000;
endcase
endmodule

```

```

module regn3(R, L, Clock, Q);
parameter n = 6;
input [n-1:0] R;
input L, Clock;
output[n-1:0] Q;
reg [n-1:0] Q;
always @(posedge Clock)
if (L)
Q <= R;
Endmodule

```

OUTPUT :

